 


Question 0)



Front-end tool: *yosys*. Its job is to parse the Verilog RTL, elaborate the design hierarchy, and synthesize it into an internal mathematical representation (like an Abstract Syntax Tree (AST Representation) or a mapped netlist).

Back-end verification engine & Reasoning engine: *ABC* or the built-in Yosys *sat* command. The reasoning engine running inside them is a **SAT Solver** (like MiniSAT or Z3).

Mathematical Model: A mathematical model is an abstract representation of the hardware's behavior over time using logic formulas and state variables.

- *Example to give:* A **Kripke Structure** or a Finite State Machine (FSM). It is defined as a tuple (S, S_0, R, L) , where S is the set of all possible states, S_0 is the initial state, R is the transition relation (next-state logic), and L tracks the outputs.
- Other example from class is BDD or BMC

SAT for Equivalence vs. BMC:

- *Equivalence:* The SAT solver checks if a "Miter" circuit (two circuits XORed together) can ever output a 1.
- *BMC (Bounded Model Checking):* The SAT solver unrolls the design for k clock cycles and checks if a specific property violation can occur within those k steps.

Output of the Solver:

- **SAT (Satisfiable):** The solver found a valid path. In equivalence checking, this means a difference was found (they are NOT equivalent). In property checking, it means a counter-example was found (a bug exists).
- **UNSAT (Unsatisfiable):** The solver proved it is impossible. In equivalence, it means the circuits ARE equivalent. In property checking, it means the property holds true (no bug found).

Question 1)

Question 1. Equivalence checking

You are given two Verilog modules:

Circuit A (reference)

```
module ref(input clk, input a, input b, output reg y);
always @(posedge clk)
  y <= a & b;
endmodule
```

Circuit B (implementation)

```
module impl(input clk, input a, input b, output reg y);
always @(posedge clk)
  y <= ~(~a | ~b);
endmodule
```

Simulation

Using ABC (via Yosys):

Check whether both circuits are **sequentially equivalent**

Give a description of each command you have used for formal verification

Theoretical Work

Model both circuits as transition systems

Construct a miter circuit:

Using SAT-based sequential equivalence checking, determine whether:

$$M_1 \equiv M_2$$

```
read_verilog circuit_1.v
```

```
read_verilog circuit_2.v
```

```
proc
```

```
opt
```

```
equiv_make ref imp equiv_miter
```

```
hierarchy -top equiv_miter
```

```
flatten
```

```
equiv_simple
```

```
equiv_induct
```

```
equiv_status -assert
```

Output :

```
169 Removing unused module `Ver`.
170 Removed 2 unused modules.
171
172 7. Executing FLATTEN pass (flatten design).
173
174 8. Executing EQUIV_SIMPLE pass.
175 Found 1 unproven $equiv cells (1 groups) in equiv_miter:
176   Trying to prove $equiv for `y`: failed.
177 Proved 0 previously unproven $equiv cells.
178
179 9. Executing EQUIV_INDUCT pass.
180 Found 1 unproven $equiv cells in module equiv_miter:
181   Proving existence of base case for step 1. (78 clauses over 35 variables)
182   Proving induction step 1. (173 clauses over 74 variables)
183   Proof for induction step holds. Entire workset of 1 cells proven!
184 Proved 1 previously unproven $equiv cells.
185
186 10. Executing EQUIV_STATUS pass.
187 Found 1 $equiv cells in equiv_miter:
188   Of those cells 1 are proven and 0 are unproven.
189   Equivalence successfully proven!
190
191 End of script. Logfile hash: 686824a361, CPU: user 0.02s system 0.01s, MEM: 9.20 MB peak
192 Yosys 0.33 (git sha1 2584903a060)
193 Time spent: 30% 4x opt_expr (0 sec), 19% 3x opt_merge (0 sec), ...
```

Question 2)

Question 2. Property checking –BMC using SAT solver

Given a counter:

```
module counter(input clk, input rst, output reg [1:0] count);
always @(posedge clk) begin
  if (rst)
    count <= 2'b00;
  else
    count <= count + 1;
end
endmodule
```

Simulation

Property to Verify Safety property

The counter should never reach state 11

$G \neg (count = 2'b11)$

Theoretical work

Apply Bounded Model Checking (BMC)

Construct SAT formula:

Give a description of each command you have used for formal verification

In Verilog code have you added anything for property check?

```
read_verilog -sv -D FORMAL countersques.v
```

```
prep -top counter
```

```
sat -verify -prove-asserts -seq 5 -show-inputs -show-outputs -show-regs
```

RTL :

```
module counter(input clk, input rst, output reg [1:0] count);
```

```
  always @(posedge clk) begin
```

```
    if (rst)
```

```
      count <= 2'b00;
```

```
    else
```

```
      count <= count + 1;
```

```
  end
```

```
`ifdef FORMAL
```

```
  always @(posedge clk) begin
```

```
    // The property: The counter should never reach state 11
```

```

220 Import show expression: \count
221 Import show expression: $formal$countersqes.v:11$1_EN
222 Import show expression: $formal$countersqes.v:11$1_CHECK
223
224 Solving problem with 249 variables and 629 clauses..
225 SAT proof finished - model found: FAIL!
226
227      _____
228      (____\          /___)   /___)   (__)|         |__|
229      _____)_____ _-_|_|_ _-_|_|_ _-_|_|_ _-_|_|
230      | ____/_ ___)-\_/_(- __)(- __)|_||||_|_|_|/_-_|_|
231      |||_|_|_|_|_|_|_|_|_|_|_|_|/_-_|_|_|_|_|_|_|_|_|_|
232      |_|_|_|_|_\_/_\_/_|_|_|_|_|_|_|_|_|_|_|_|_|_|_|_|_|
233
234
235 Time Signal Name                               Dec       Hex       Bin
236 -----
237 init $formal$countersqes.v:11$1_CHECK           0         0         0
238 init $formal$countersqes.v:11$1_EN              0         0         0
239 init \count                                       0         0        00
240 -----
241 1 $formal$countersqes.v:11$1_CHECK               0         0         0
242 1 $formal$countersqes.v:11$1_EN                 0         0         0
243 1 \clk                                             0         0         0
244 1 \count                                           0         0        00
245 1 \rst                                             0         0         0
246 -----
247 2 $formal$countersqes.v:11$1_CHECK               1         1         1
248 2 $formal$countersqes.v:11$1_EN                 1         1         1
249 2 \clk                                             0         0         0
250 2 \count                                           1         1        01
251 2 \rst                                             0         0         0
252 -----
253 3 $formal$countersqes.v:11$1_CHECK               1         1         1
254 3 $formal$countersqes.v:11$1_EN                 1         1         1
255 3 \clk                                             0         0         0
256 3 \count                                           2         2        10
257 3 \rst                                             0         0         0
258 -----
259 4 $formal$countersqes.v:11$1_CHECK               1         1         1
260 4 $formal$countersqes.v:11$1_EN                 1         1         1
261 4 \clk                                             0         0         0
262 4 \count                                           3         3        11
263 4 \rst                                             0         0         0
264 -----
265 5 $formal$countersqes.v:11$1_CHECK               0         0         0
266 5 $formal$countersqes.v:11$1_EN                 1         1         1
267 5 \clk                                             0         0         0
268 5 \count                                           0         0        00
269 5 \rst                                             1         1         1
270
271 ERROR: called with -verify and proof did fail!
272 amrut@maverick:~/yosys/examples/cmos$

```

Question 3)

Question 3. Property checking –BMC using SAT solver

For the same 2 bit counter –liveness check

Property to Verify

Eventually count becomes 00 again

$GF(count = 00)$

Give a description of each command you have used for formal verification

RTL :

```
module counter(input clk, input rst, output reg [1:0] count);
```

```
    initial count = 2'b00;
```

```
    always @(posedge clk) begin
```

```
        if (rst)
```

```
            count <= 2'b00;
```

```
        else
```

```
            count <= count + 1;
```

```
    end
```

```
    `ifdef FORMAL
```

```
        reg [2:0] cycles_since_zero;
```

```
        initial cycles_since_zero = 0;
```

```
        always @(posedge clk) begin
```

```
    if (rst || count == 2'b00) begin
        cycles_since_zero <= 0;
    end else begin
        cycles_since_zero <= cycles_since_zero + 1;
    end

    assert(cycles_since_zero < 4);
end
`endif
endmodule
```

Yosys;

```
read_verilog -sv -D FORMAL counter_live.v
```

```
prep -top counter
```

```
sat -verify -prove-asserts -seq 8 -show-regs
```

Output :

```
65 Import show expression: $formal$counter_live.v:24$1_CHECK
66 Import show expression: \cycles_since_zero
67
68 Solving problem with 929 variables and 2453 clauses..
69 SAT proof finished - no model found: SUCCESS!
70
71
72      /$$$$$      /$$$$$$$      /$$$$$$$
73      /$__ $$      | $$_____/      | $$__ $$
74      | $$ \ $$      | $$          | $$ \ $$
75      | $$ | $$      | $$$$$$      | $$ | $$
76      | $$ | $$      | $$____/      | $$ | $$
77      | $$/$$ $$      | $$          | $$ | $$
78      | $$$$$$/ /$$| $$$$$$$$ /$$| $$$$$$/ /$$
79      \___ $$$|_/_|_____/|_/_|_____/|_/_/
80      \_/_
81
82 End of script. Logfile hash: af0809eaf1, CPU: user 0.03s system 0.01s, MEM: 10.41 MB peak
83 Yosys 0.33 (git sha1 2584903a060)
84 Time spent: 31% 1x sat (0 sec), 20% 5x opt_expr (0 sec), ...
85 amrut@Maverick:~/yosys/examples/cmos$
```


Question 4)

Question 4. Optimization and equivalence check

To perform logic optimization on a given RTL design and verify that the optimized netlist is functionally equivalent to the original design using formal equivalence checking.

```
module top(input A, B, C, output F);  
  assign F = (A & B) | (A & B & C);  
endmodule
```

Part A: Logic Optimization

Write a Yosys script to:

Read the RTL file

Prepare the design

Perform logic optimization

Generate the optimized netlist

Give a description of each command you
have used for formal verification

Part B: Equivalence Checking

Write another Yosys script to:

Load the original RTL

Load the optimized netlist

Create a miter circuit

Perform equivalence checking

ECS324 VLSI TESTING AND VERIFICATION

Yosys to make netlist :

```
read_verilog ques4.v
```

```
prep -top top
```

```
opt
```

```
write_verilog top_opt.v
```

Yosys to do equiv check : (very similar to question 1)

```
read_verilog ques4.v
```

```
rename top top_ref
```

```
read_verilog top_opt.v
```

```
rename top top_impl
```

```
equiv_make top_ref top_impl equiv_miter
```

```
hierarchy -top equiv_miter
```

```
equiv_simple
```

```
equiv_status -assert
```

Output :

```
308
309 4. Executing HIERARCHY pass (managing design hierarchy).
310
311 4.1. Analyzing design hierarchy..
312 Top module: \equiv_miter
313
314 4.2. Analyzing design hierarchy..
315 Top module: \equiv_miter
316 Removing unused module \top_impl'.
317 Removing unused module \top_ref'.
318 Removed 2 unused modules.
319
320 5. Executing EQUIV_SIMPLE pass.
321 Found 1 unproven $equiv cells (1 groups) in equiv_miter:
322   Trying to prove $equiv for \F: success!
323   Proved 1 previously unproven $equiv cells.
324
325 6. Executing EQUIV_STATUS pass.
326 Found 1 $equiv cells in equiv_miter:
327   Of those cells 1 are proven and 0 are unproven.
328   Equivalence successfully proven!
329
330 End of script. Logfile hash: f617e5e869, CPU: user 0.01s system 0.01s, MEM: 8.85 MB peak
331 Yosys 0.33 (git sha1 2584903a060)
332 Time spent: 35% 4x read_verilog (0 sec), 28% 1x equiv_make (0 sec), ...
333 amrut@Maverick:~/yosys/examples/cmos$
```